

rk2log

Deriving the transfer function for a bridged t-network pt. 1

This post will derive the transfer function for a [bridged t-network](#), expressed using impedances, and will be the first of a series of posts I'll be making as I'm learning about, and working on, a design for an analog drum machine similar to that of the famous Roland machines.

The post will begin with a short background for why the bridged t-network in particular will be examined. Then, the derivation of the transfer function will be given, followed by a simulation of the circuit to validate that the derived expression is correct.

I. Background

In the [service manual](#) for the tr-808 drum machine, the following principal diagram for the basic pulse-triggered sound generator can be found:

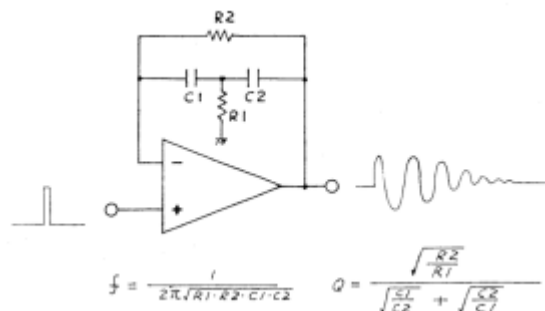


Fig 1, representative bridged t-network schematic from tr-808 service manual

While the circuitry in the tr-808 is not as straight forward as in Fig 1, it is an excellent starting point for a study. By understanding the principal schematic, it creates the

foundation for learning about the more complex and nuanced circuits in the actual hardware.

The sound generator consists of an operational amplifier (op-amp) and a feedback circuit consisting of the bridged t-network, which forms a bandpass filter with a high resonance. The filter acts as a damped oscillator (see Fig 2), and will self-oscillate at the resonance-frequency for a short time after being stimulated by an input-pulse. This makes up the basic drum sound.

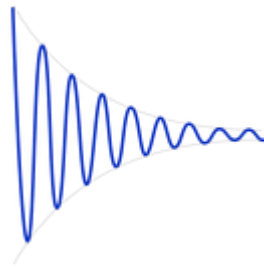


Fig 2, example of a damped oscillation

The circuit above (Fig 1) will be able to create a tom-like sound or a kick-like sound depending on the resonant frequency's value, which is determined by the values of the circuit components.

II. Transfer function for the bridged t-network

The transfer function describes the relation between the components and the circuits' behavior, and will be derived from the following diagram:

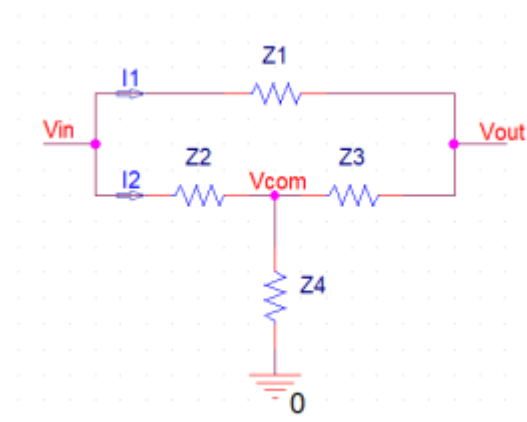


Fig 3, bridged t-network with currents labeled I_1 and I_2

The transfer function is an expression for the ratio between the output voltage V_o and a given input voltage V_i :

$$\text{transfer function} = \frac{V_o}{V_i}$$

Deriving the transfer function from the schematic becomes a process of finding an expression for the output voltage as a function of the input voltage, and factoring that expression.

The output voltage node and input voltage node are separated by the impedance Z_1 . The current I_1 via Z_1 causes a voltage drop, so that the output voltage can be expressed by:

$$V_o = V_i - I_1 Z_1$$

I_1 can be expressed by introducing a common-voltage V_{com} at the junction between Z_2 , Z_3 and Z_4 :

$$I_1 = \frac{V_i - V_{com}}{Z_1 + Z_3}$$

To express the common-voltage we notice that Z_1 , Z_2 and Z_3 form an equivalent resistor $Z_{(1+3)/2}$ that together with Z_4 form a voltage divider with V_{com} as its output:

$$V_{com} = V_i \frac{Z_4}{Z_{tot}}$$

where the total impedance Z_{tot} is:

$$Z_{tot} = Z_{(1+3)/2} + Z_4$$

The current I_1 can now be rewritten as:

$$\begin{aligned}
 I_1 &= V_i \frac{1}{Z_1 + Z_3} - V_{com} \frac{1}{Z_1 + Z_3} \\
 &= V_i \frac{1}{Z_1 + Z_3} - V_i \frac{Z_4}{Z_{tot}} \frac{1}{Z_1 + Z_3}
 \end{aligned}$$

and then factored:

$$\begin{aligned}
 &= \frac{V_i}{Z_1 + Z_3} \left(1 - \frac{Z_4}{Z_{tot}} \right) \\
 &= \frac{V_i}{Z_1 + Z_3} \left(\frac{Z_{tot} - Z_4}{Z_{tot}} \right) \\
 &= \frac{V_i}{Z_1 + Z_3} \left(\frac{Z_{(1+3)/2}}{Z_{tot}} \right)
 \end{aligned}$$

By calculating the equivalent impedance $Z_{(1+3)/2}$ and then Z_{tot} , the expression for the current can be made explicit:

$$\begin{aligned}
 Z_{(1+3)/2} &= \frac{(Z_1 + Z_3)Z_2}{(Z_1 + Z_3) + Z_2} \\
 Z_{tot} &= \frac{(Z_1 + Z_3)Z_2}{(Z_1 + Z_3) + Z_2} + Z_4 \\
 &= \frac{(Z_1 + Z_3)Z_2}{Z_1 + Z_2 + Z_3} + Z_4 \frac{(Z_1 + Z_2 + Z_3)}{(Z_1 + Z_2 + Z_3)} \\
 &= \frac{(Z_1 + Z_3)Z_2 + Z_4(Z_1 + Z_2 + Z_3)}{Z_1 + Z_2 + Z_3}
 \end{aligned}$$

The impedance-quotient then becomes:

$$\begin{aligned}
 \frac{Z_{(1+3)/2}}{Z_{tot}} &= \frac{\frac{(Z_1 + Z_3)Z_2}{Z_1 + Z_2 + Z_3}}{\frac{(Z_1 + Z_3)Z_2 + Z_4(Z_1 + Z_2 + Z_3)}{Z_1 + Z_2 + Z_3}} \\
 &= \frac{(Z_1 + Z_3)Z_2}{(Z_1 + Z_3)Z_2 + Z_4(Z_1 + Z_2 + Z_3)}
 \end{aligned}$$

The current I_1 can now be expressed with the known impedances as:

$$\begin{aligned}
 I_1 &= \frac{V_i}{Z_1 + Z_3} \left(\frac{Z_{(1+3)/2}}{Z_{tot}} \right) \\
 &= \frac{V_i}{(Z_1 + Z_3)} \frac{(Z_1 + Z_3)Z_2}{(Z_1 + Z_3)Z_2 + Z_4(Z_1 + Z_2 + Z_3)} \\
 &= V_i \frac{Z_2}{(Z_1 + Z_3)Z_2 + Z_4(Z_1 + Z_2 + Z_3)}
 \end{aligned}$$

Finally, we can return to the output voltage expression, and factor out V_i :

$$\begin{aligned}
 V_o &= V_i - I_1 Z_1 \\
 &= V_i - V_i \frac{Z_2}{(Z_1 + Z_3)Z_2 + Z_4(Z_1 + Z_2 + Z_3)} Z_1 \\
 &= V_i \left(1 - \frac{Z_1 Z_2}{(Z_1 + Z_3)Z_2 + Z_4(Z_1 + Z_2 + Z_3)} \right)
 \end{aligned}$$

and then calculate the difference inside the parentheses by expanding the leading 1-term:

$$\begin{aligned}
 &= V_i \frac{(Z_1 + Z_3)Z_2 + Z_4(Z_1 + Z_2 + Z_3) - Z_1 Z_2}{(Z_1 + Z_3)Z_2 + Z_4(Z_1 + Z_2 + Z_3)} \\
 &= V_i \frac{Z_1 Z_2 + Z_2 Z_3 + Z_4(Z_1 + Z_2 + Z_3) - Z_1 Z_2}{(Z_1 + Z_3)Z_2 + Z_4(Z_1 + Z_2 + Z_3)} \\
 &= V_i \frac{Z_2 Z_3 + Z_4(Z_1 + Z_2 + Z_3)}{(Z_1 + Z_3)Z_2 + Z_4(Z_1 + Z_2 + Z_3)}
 \end{aligned}$$

With the original expression fully factorized, the transfer function can now be expressed:

$$\frac{V_o}{V_i} = \frac{Z_2 Z_3 + Z_4(Z_1 + Z_2 + Z_3)}{(Z_1 + Z_3)Z_2 + Z_4(Z_1 + Z_2 + Z_3)}$$

And the parentheses expanded:

$$\frac{V_o}{V_i} = \frac{Z_1 Z_4 + Z_2 Z_3 + Z_2 Z_4 + Z_3 Z_4}{Z_1 Z_2 + Z_1 Z_4 + Z_2 Z_3 + Z_2 Z_4 + Z_3 Z_4}$$

The transfer function for the schematic has now been derived.

III. Validating the transfer function with a simulation

In order to validate that the transfer function is correct, it will be tested using resistive values and compared to the output from the simulation software PSpice.

A simple straight forward test is to simply define all the impedances to 1kΩ:

$$\frac{V_o}{V_i}(Z_i = 1k) = \frac{(1 + 1 + 1 + 1)k}{(1 + 1 + 1 + 1 + 1)k} = \frac{4k}{5k} = 0.8$$

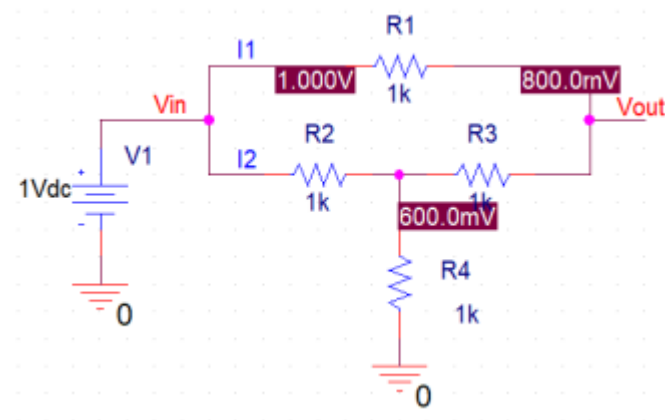


Fig 4, simulation result from PSpice for test 1

With the input voltage V_i set to 1V, the output voltage V_o is 0.8V as expected.

In order to make sure this isn't just a fluke result, another set of test-values can be defined:

$$\begin{aligned} \frac{V_o}{V_i}(V_i = ik) &= \frac{(1 \cdot 4 + 2 \cdot 3 + 2 \cdot 4 + 3 \cdot 4)k}{(1 \cdot 2 + 1 \cdot 4 + 2 \cdot 3 + 2 \cdot 4 + 3 \cdot 4)k} \\ &= \frac{4 + 6 + 8 + 12}{2 + 4 + 6 + 8 + 12} = \frac{30}{32} = 0.9375 \end{aligned}$$

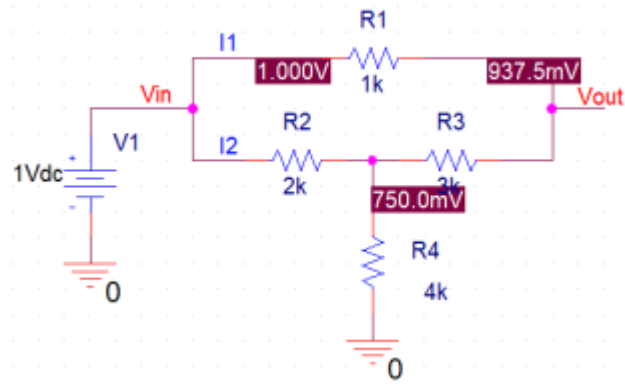


Fig 5, simulation result from PSpice for test 2

For this second test the result is also the expected one, with an input voltage V_i of 1 giving 937.5 mV output.

IV. Conclusion

A valid transfer function for the bridged t-network has been derived for impedances. In order to analyze its oscillation properties and bode diagram, those impedances need to be defined using resistors R and capacitors C .









This will be explored in the next part.

Advertisements

AUTOMATTIC

**We're hiring
backend developers.
Join us!**

[APPLY](#)

REPORT THIS AD

**Earn money from
your WordPress site**

WordAds

SIGN UP

REPORT THIS AD

Share this:



Twitter



Facebook



Google

Like

Be the first to like this.

**Author: rk2log**I make some stuff and write about it. [View all posts by rk2log](#)

June 3, 2018 / Uncategorized

One thought on “Deriving the transfer function for a bridged t-network pt. 1”

**HC**

February 7, 2019 at 9:26 am

Thanks dude

[Like](#)

rk2log /